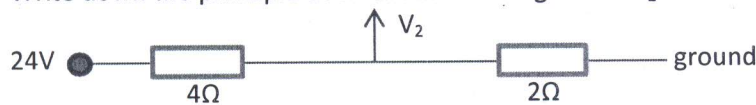



- A4. a) Write down the principle of wheat-stone bridge. Find V_2 of the following network

$3\frac{2}{3}$




- b) Using the principle of Superposition, find the current I_2 through 12K resistor

4

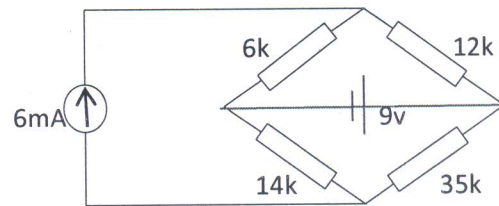

- c) Design a low-pass active filter as shown below with a dc gain of 4 and a corner frequency of 500Hz. Given $C_f = 0.2\mu F$.

4

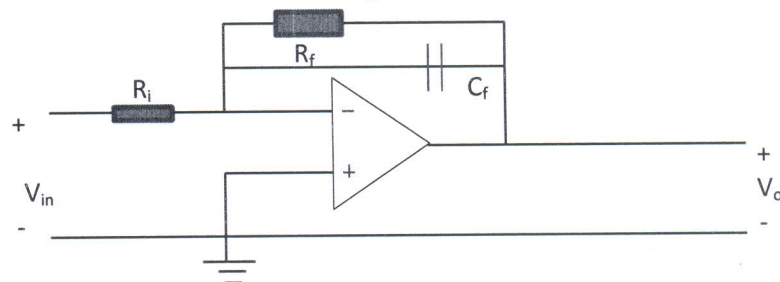

Section B

- B1. a) What is CRO? Explain the working principle of an oscilloscope with proper diagram.
 b) What do you mean by avo-meter? What are quantities those can be measured using avo-meter and how?
 c) What do you mean by constant-k filter?

3

$5\frac{2}{3}$

3

- B2. a) What do you mean by Lissajous Patterns? Why it is used?

$3\frac{2}{3}$


- b) During electrostatic deflection in an oscilloscope, the displacement in y-direction is $y = \frac{1}{2} \frac{eE_y}{m \cdot V_{0x}^2} \cdot x^2$

5

using the information prove that the deflection $D = \frac{L e E_d l_d}{m \cdot d V_{0x}^2}$

- c) Find the frequency of the vertical plates if the frequency applied to horizontal Plate is 50Hz for the patterns shown in first and second figure.

3

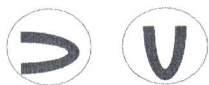

- B3. a) What is m-derived section? Show that for a m-derived section $\omega_c = \frac{\omega_c}{\sqrt{1-m^2}}$
 b) Determine the transfer function and cut-off frequencies for an active band-pass filter.
 c) Design a notch filter considering the value of $\omega_0 = 20Krad/s$, $K=5$ and $Q=10$. Assume $R=R_i = 10K\Omega$

4

$3\frac{2}{3}$

4

- B4. a) Write short note(any two) i) P^H meter ii) thermostats iii) Spectrophotometer

4

- b) Show that, for symmetrical two part network, terminal impedance is $\sqrt{\frac{B}{C}}$ (where B,C = two port parameter)

5

- c) What is the difference band pass and band-reject filter?


$2\frac{2}{3}$

Answer any three from each section on separate script marked A and B.


Section-A

- A1. a) Define node, junction, loop and mesh from circuit diagram and also identify it.
b) Draw the norton's network from the following fig

3
4₃

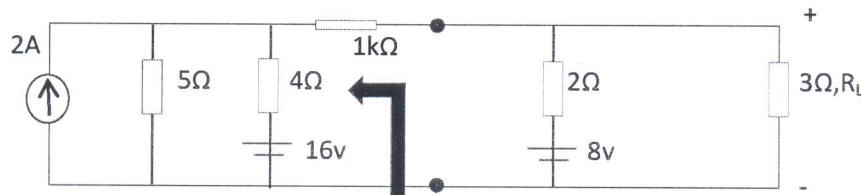

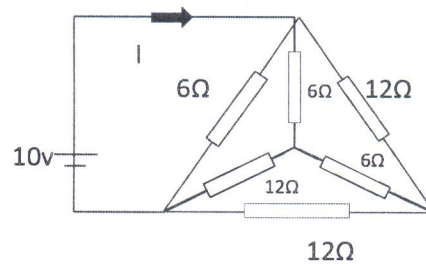
- c) Find the resistance R_T and I from the circuit



4

- A2. a) Find the Thevenin equivalent circuit to the left of the terminal a-b. then find the current through $R_L=6, 16$ and 36Ω .

6

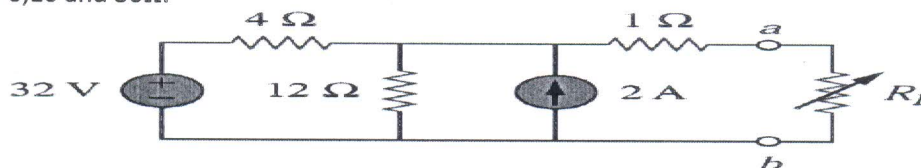


- b) Derive the condition for which maximum power will be transferred to the receiving terminal. At this condition Prove that efficiency of this system is 50%.
c) State and Explain Nortons Theorem.

3₃

2

- A3. a) Solve the fig by using nodal equation

4₃

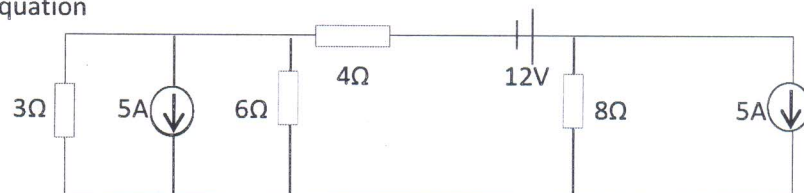

- b) For the network shown in Fig Q1(b), find the branch currents I_1 and I_2 also find current through R_2 .

4

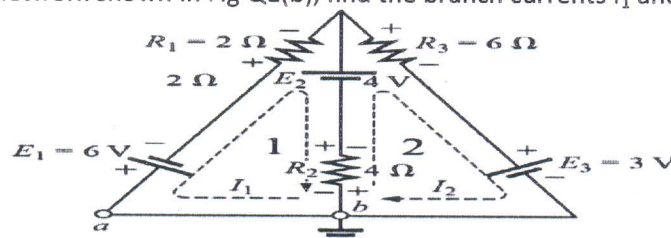


Fig. Q.1(b)

- c) Prove that the following circuit satisfying the reciprocity theorem.

3

