

Bangabandhu Sheikh Mujibur Rahman Science & Technology University, Gopalganj.
Department of Computer Science and Engineering
1st Year 2nd Semester B. Sc. Engineering Examination-2013
Course: CSE160 (Introduction to Digital Electronics)

Full Marks: 70

Time: 3 hours

N.B.: Instruction for Candidates:

- i) The figures in the right margin indicate full marks.
- ii) Answer any **SIX** questions, taking any **THREE** from each section.
- iii) Use separate answer script for each section.

Section - A

1. a) Subtract $(01101)_2$ from $(11011)_2$ using 1st complement method. 3
b) Use 2's complement method to subtract $(1101)_2$ from $(1010)_2$. 3
c) What is a logic gate? Why NOR and NAND gates are called universal gate? 5.67

2. a) What do you mean minterm and maxterm? 3
b) Simplify the following expression to a minimum number of gates: 3
i) $ABC + \bar{A}B + AB\bar{C} + AC$
ii) $\bar{A}B(\bar{D} + CD) + B(A + \bar{A}CD)$
c) Minimize the following switching function using Quine –McClusky method: 5.67
$$f(w, x, y, z) = \sum m(0,1,2,4,5,6,8,9,12,13,14)$$

3. a) State and Prove De-Morgan's theorem. 3
b) What are the advantages of encoding a decimal number in BCD rather than in straight binary number? What is a disadvantage? 2
c) State the steps involved in Gray to binary conversion. Convert the gray code 10101101 into its binary equivalent. 3
d) Design a logic circuit that has three inputs A, B and C, and whose output will be HIGH only when a majority of the inputs are high. 3.67

4. a) Describe TTL low state circuit operation with appropriate figure. 5
b) Given $I_{OL} = 8 \text{ mA}$, $I_{IL} = 0.2 \text{ mA}$, $I_{OH} = 0.5 \text{ mA}$ and $I_{IH} = 22 \mu\text{A}$. Drive fan-out at different state. 2
c) Draw the circuit diagram and truth table of a CMOS NAND gate. 4.67

8/12

Section - B

5. a) Prove the following Boolean identities: 5
 i) $(A + B)(A + C) = A + BC$
 ii) $A + \bar{A}B = A + B$
 b) Design and draw the circuit diagram of full subtractor. 4.67
 c) Simplify the expression: $(AB + C)(AB + D)$. 2
6. a) What do you mean by a number system? 2
 b) Discuss hexadecimal number system. 3
 c) Convert 4
 i) $(777)_8$ to decimal
 ii) $(10101.11)_2$ to octal
 iii) $(43.875)_{10}$ to hexadecimal
 iv) $(11001.101)_2$ to decimal
 d) What is CMOS technology? What are the advantages of it? 2.67
7. a) Design a logic circuit for expression: $F = A(B + CD) + B\bar{C}$ 5
 i) Using NAND gates only.
 ii) Using NOR gates only.
 b) What are called don't care conditions? 2
 c) To simplify the following switching function using K-map and draw logic circuit. 4.67

$$F(a, b, c, d) = \sum m(0, 2, 6, 8, 12, 13, 15) + d(3, 9, 10)$$
8. a) What do you mean by digital ICs? Describe different levels of ICs based on complexity. 3
 b) What are bipolar and unipolar digital ICs? What is the main advantage of CMOS over TTL? 2
 c) Draw the figure for input voltage ranges for TTL and CMOS. 2
 d) What is fan-out? What do you mean by propagation delay? Explain with example. 2.67
 e) Given $V_{OL} = 0.3$, $V_{IL} = 0.8$, $V_{OH} = 2.6$ and $V_{IH} = 1.8$. Find out maximum amplitude noise spike at high and low output are driving an input. 2